

Tribhuvan University
Institute of Science and Technology

2074



Bachelor Level / First Year/ First Semester/ Science
Computer Science and Information Technology (CSc. 111)
(Digital Logic)


Full Marks: 60
Pass Marks: 24
Time: 3 hours.

*Candidates are required to give their answers in their own words as far as practicable.
The figures in the margin indicate full marks.*

Attempt any two questions:

(2×10=20)

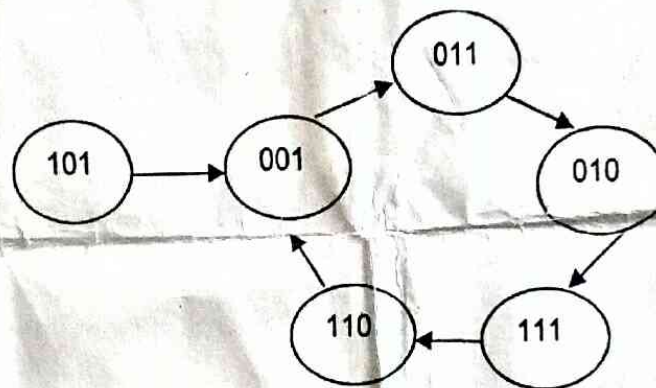1. Implement the following function $F = \sum (0, 3, 5, 6, 7)$ using
 - (a) Decoder
 - (b) Multiplexer
 - (c) PLA
2. Differentiate between PAL and PLA. Design a counter as shown in the state diagram below



3. Draw a block diagram, truth table and logic circuit of 1*16 Demultiplexer and explain its working principle.

Attempt any eight questions:

(8×5=40)

4. Perform the arithmetic operation $(+42)+(-13)$ and $(-42)-(-13)$ in binary using the signed -2's-complement representation for negative numbers.

5. Express the complement of the following function in sum of minterms.
 $F(A, B, C, D) = \sum(0, 2, 6, 11, 13, 14)$

6. Reduce the following function using k-map
 $F = wxy + yz + xy'z + x'y$

7. Design a combinational circuit with three inputs and six outputs. The output binary number should be the square of the input binary number.

8. Design a 5×32 decoder with four 3×8 decoder with enable and one 2×4 decoder. Use block diagrams only.

CSc.111-2074 ☆

9. Design and explain the Decimal adder with truth table and suitable diagram.
10. Explain shift register with parallel load. Highlight on its practical implications.
11. Explain master slave J-K flipflop.
12. Write short notes on (**any two**):
 - (a) State diagram
 - ✓(b) De-Morgan's theorem
 - (c) TTL