

**Digital Logic**

**2068**

Full Marks : 60

Pass Marks : 24

Time : 3 hrs.

**Long answer questions :**

**Attempt any two questions :**

**(2\*10=20)**

- 1.) Draw a block diagram truth table and logic circuit of 1\*16 Demultiplexer and explain its working principle.
- 2.) Design a 3 bit synchronous counter and explain it.
- 3.) What is magnitude comparator? Design a logic circuit for 4 bit comparator and explain it.

**Short answer questions :**

**Attempt any eight questions :**

**(8\*5=40)**

- 4.) Design a half subtractor circuit using only NAND gates.
- 5.) Convert the following decimal numbers into Hexadecimal and Octal numbers:
  - a.) 504
  - b.) 250
- 6.) Design an encoder using universal gates.
- 7.) What do you mean by D-flip-flop?
- 8.) What is sequential logic? What are the important features?
- 9.) Simplify the Boolean function using K-Maps.  
$$F = X'yz + X'yz' + Xy'z' + Xy'z$$
- 10.) Draw a parallel-parallel-out shift register and explain it.
- 11.) Explain the 4 bit ripple counter.
- 12.) Explain the programmable logic array.
- 13.) Write short notes on :
  - a.) Asynchronous counter
  - b.) Multiplexers
  - c.) State reduction table